

ARITHMETIC CIRCUITS **SIMULATION USING VERILOG**

NAME :ATHISH S A

ROLL NO: B21EC040

RIPPLE CARRY ADDER:

CODE:

```
module ripple_carry_adder(input [3:0] A, B,  
    input Cin,  
    output [3:0] S,  
    output Cout);  
    wire [3:0] sum;  
    wire c1, c2, c3;  
  
    full_adder fa1(.a(A[0]), .b(B[0]), .c(Cin), .sum(sum[0]), .cout(c1));  
    full_adder fa2(.a(A[1]), .b(B[1]), .c(c1), .sum(sum[1]), .cout(c2));  
    full_adder fa3(.a(A[2]), .b(B[2]), .c(c2), .sum(sum[2]), .cout(c3));  
    full_adder fa4(.a(A[3]), .b(B[3]), .c(c3), .sum(sum[3]), .cout(Cout));  
  
    assign S = sum;  
endmodule  
  
module full_adder(input a, b, c,  
    output sum, cout);  
    assign {cout, sum} = a + b + c;  
endmodule
```

TEST BENCH CODE:

```
module ripple_carry_adder_tb;
```

```

reg [3:0] A, B;
reg Cin;

wire [3:0] S;

wire Cout;

ripple_carry_adder rca(.A(A), .B(B), .Cin(Cin), .S(S),
.Cout(Cout));

initial begin

$monitor("A=%b, B=%b, Cin=%b, S=%b, Cout=%b", A, B, Cin, S, Cout);

A = 4'b0000;
B = 4'b0000;
Cin = 1'b0;
#5;

A = 4'b0001;
B = 4'b0001;
Cin = 1'b0;
#5;

A = 4'b0111;
B = 4'b0110;
Cin = 1'b0;
#5;

A = 4'b1111;
B = 4'b1111;
Cin = 1'b0;
#5;

A = 4'b0110;
B = 4'b0101;

```

```
Cin = 1'b1;
#5;
```

```
$finish;
```

```
end
```


```
initial begin
```

```
$dumpfile("dump.vcd");
```


```
$dumpvars(1);
```

```
end
```

```
endmodule
```

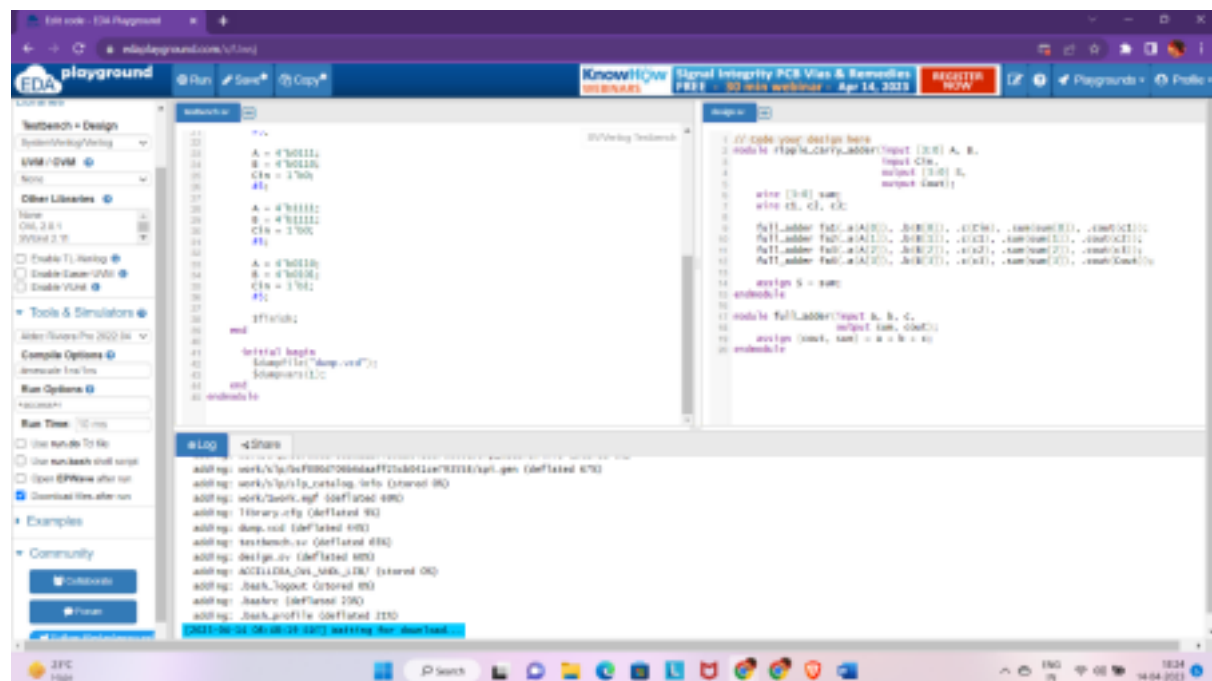

EP WAVE:

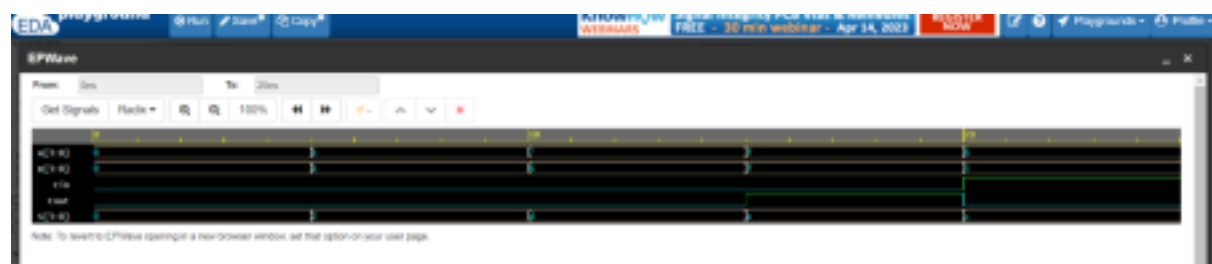

BINARY RESTORING ADDITION:

CODE:

```
module binary_restoring_division(dividend, divisor, quotient, remainder, clk,  
rst); parameter WIDTH = 8; // change WIDTH to match the size of the operands
```

```
input signed [WIDTH-1:0] dividend;  
input signed [WIDTH-1:0] divisor;  
output signed [WIDTH-1:0] quotient;  
output signed [WIDTH-1:0] remainder;  
input clk, rst;
```

```
reg signed [WIDTH-1:0] dividend_reg;  
reg signed [WIDTH-1:0] divisor_reg;  
reg signed [WIDTH-1:0] quotient_reg;  
reg signed [WIDTH-1:0] remainder_reg;  
reg [1:0] state;  
reg signed [WIDTH-1:0] temp;
```

```
always @(posedge clk) begin
```

```
if (rst) begin
```

```
state <= 2'b00;
```

```
dividend_reg <= 0;
```

```
divisor_reg <= 0;
```

```
quotient_reg <= 0;
```

```
remainder_reg <= 0;
```

```
end
```

```
else begin
```

```
case (state)
```

```
2'b00: begin // initialize
```

```
dividend_reg <= dividend;
```

```
divisor_reg <= divisor;
```

```
state <= 2'b01;
```

```

end

2'b01: begin // check sign
if (dividend_reg[WIDTH-1] == divisor_reg[WIDTH-1])
state <= 2'b10;

else
state <= 2'b11;

end

2'b10: begin // subtract divisor
temp <= dividend_reg - divisor_reg;
if (temp[WIDTH-1] == dividend_reg[WIDTH-1])
quotient_reg[WIDTH-1] <= 1;
divisor_reg <= divisor_reg >> 1;
if (temp[WIDTH-1] == dividend_reg[WIDTH-1])
dividend_reg <= temp;
state <= 2'b01;
end

2'b11: begin // add divisor
temp <= dividend_reg + divisor_reg;
if (temp[WIDTH-1] != dividend_reg[WIDTH-1])
quotient_reg[WIDTH-1] <= 1;
divisor_reg <= divisor_reg >> 1;
if (temp[WIDTH-1] != dividend_reg[WIDTH-1])
dividend_reg <= temp;
state <= 2'b01;
end

endcase

end

end

```

```
assign quotient = quotient_reg;
assign remainder = dividend_reg;

endmodule
```

TEST BENCH CODE:

```
module binary_restoring_division_tb;

parameter WIDTH = 8; // change WIDTH to match the size of the operands

reg signed [WIDTH-1:0] dividend;
reg signed [WIDTH-1:0] divisor;
wire signed [WIDTH-1:0] quotient;
wire signed [WIDTH-1:0] remainder;
reg clk, rst;

binary_restoring_division dut(.dividend(dividend), .divisor(divisor), .quotient(quotient),
    .remainder(remainder), .clk(clk), .rst(rst));

initial begin
dividend = 16;
divisor = 3;
clk = 0;
rst = 1;
#10 rst = 0;
#10 dividend = -32;
#10 divisor = -4;
#10 dividend = 12;
#10 dividend = 0;
#10 dividend = -5;
#10 $finish;
end
```

```
always #5 clk = ~clk;  
initial begin
```

```
$dumpfile("binary_restoring_division_tb.vcd");
```

```
$dumpvars(0, binary_restoring_division_tb);
```

```
#10;
```

```
$pwave("dividend divisor quotient remainder\n");
```


```
end
```

```
always @* begin
```


```
$fdisplay(1, "%d %d %d %d\n", dividend, divisor, quotient, remainder);
```

```
end
```

```
endmodule
```

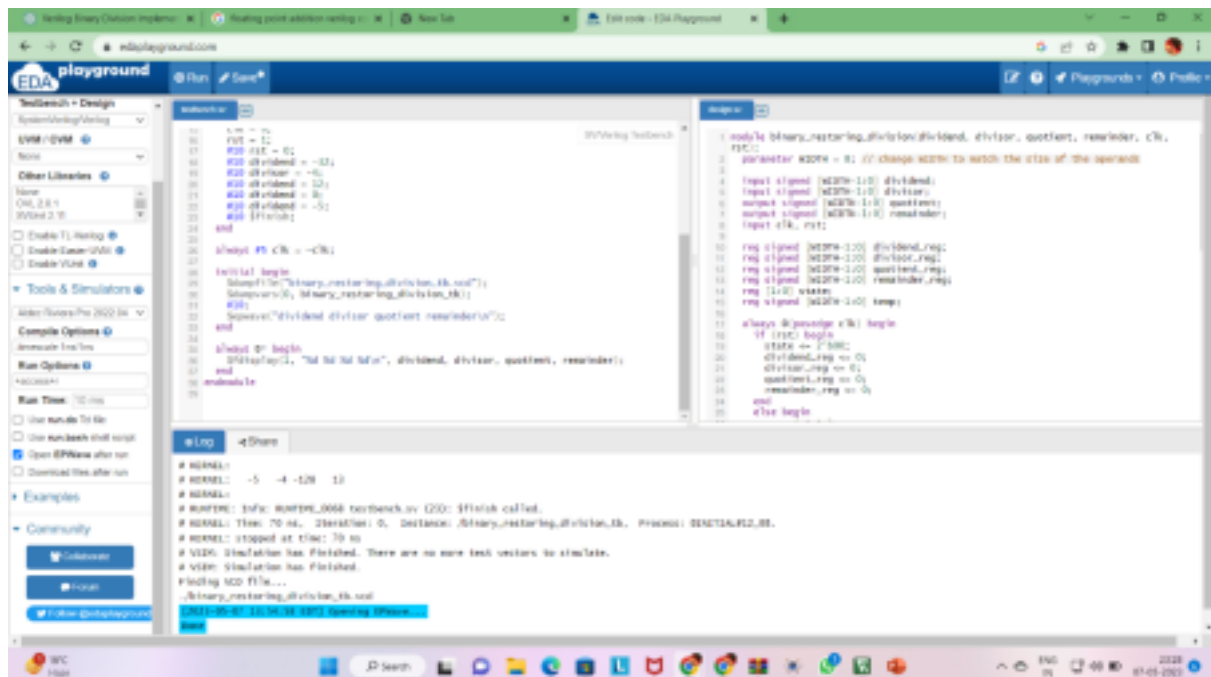

EPWAVE:

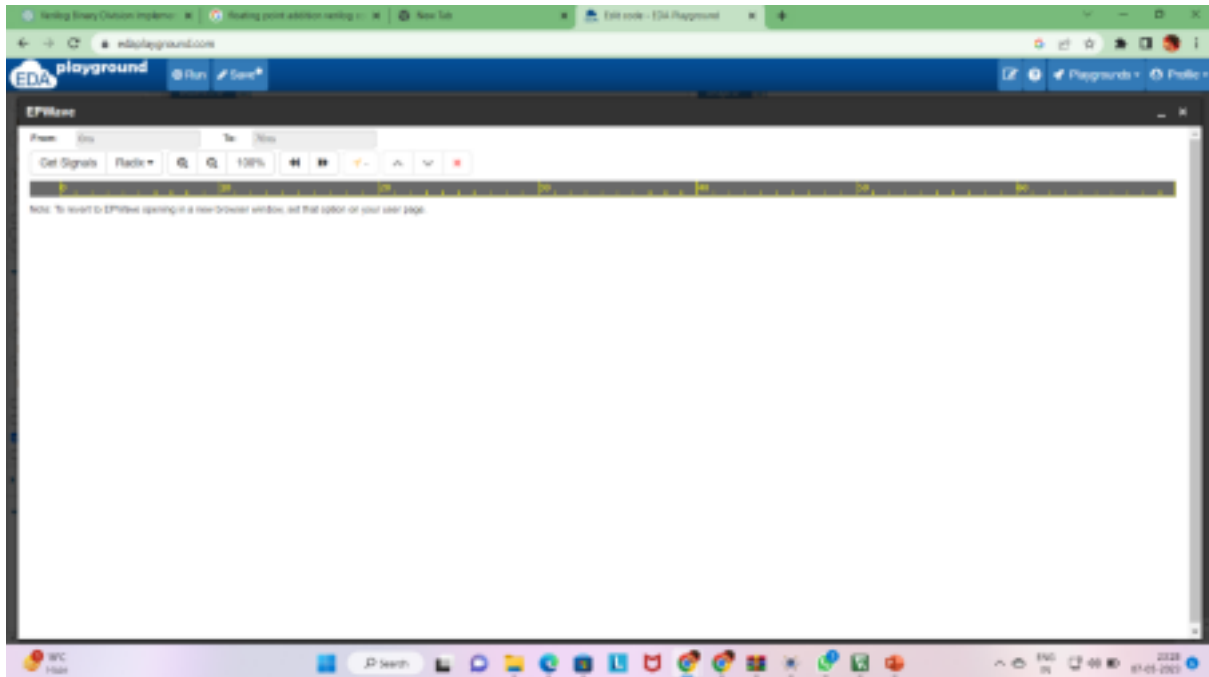

NON RESTORING DIVISION:

CODE:

```
module non_restoring_division(clk, dividend, divisor, quotient, remainder,  
state);
```

```
input clk;
```

```
input [3:0] dividend;
```

```
input [3:0] divisor;
```

```
output reg [3:0] quotient;
```

```
output reg [3:0] remainder;
```

```
output reg [1:0] state;
```

```
reg [3:0] A, S;
```

```
reg [3:0] Q;
```

```
reg [1:0] count;
```



```
always @(posedge clk)
begin
    if (count == 0)
    begin
        A <= dividend;
        S <= divisor;
        Q <= 0;
        count <= 3;
        state <= 2'b10; // shift state
    end

    else if (count == 3)
    begin
        if (A[3:0] >= S[3:0])
        begin
            A[3:0] <= A[3:0] - S[3:0];
            Q[0] <= 1;
            state <= 2'b01; // subtract state
        end

        else
        begin
            Q[0] <= 0;
            state <= 2'b10; // shift state
        end

        count <= count - 1;
    end
end
```

```
end
else
begin
A[3:0] <= (A << 1);
Q[0] <= 0;
state <= 2'b10; // shift state
count <= count - 1;
end
end
```

```
assign quotient = Q;
assign remainder = A;
endmodule
```

TEST BENCH CODE:

```
module non_restoring_division_tb();

reg clk;
reg [3:0] dividend;
reg [3:0] divisor;


wire [3:0] quotient;
wire [3:0] remainder;
wire [1:0] state;
non_restoring_division dut(clk, dividend, divisor, quotient, remainder, state);
```

```
initial
begin
    $dumpfile("non_restoring_division_tb.vcd");
    $dumpvars(0, non_restoring_division_tb);


    clk = 0;
    dividend = 4'b0001;
    divisor = 4'b0010;
    #10;
    dividend = 4'b0001;
    divisor = 4'b0011;
    #10;
    dividend = 4'b0010;
    divisor = 4'b0010;
    #10;
    dividend = 4'b1010;
    divisor = 4'b0110;
    #10;
    $stop;
end

always #5 clk = ~clk;

endmodule
```

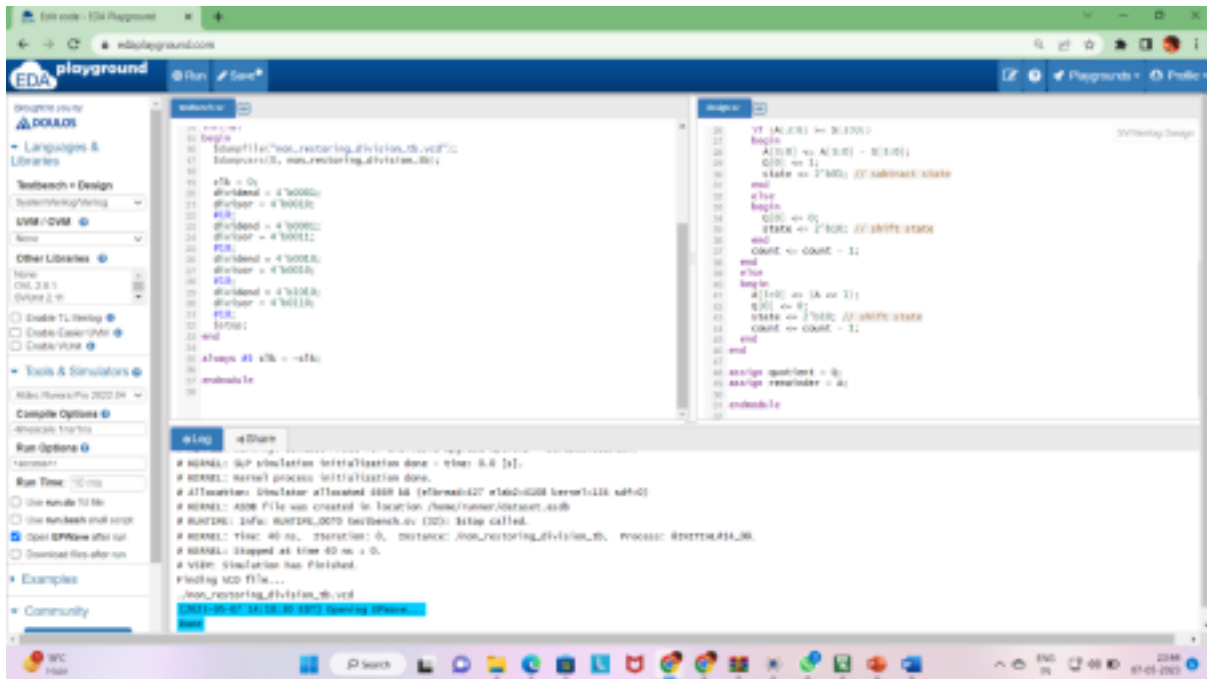

EPWAVE:

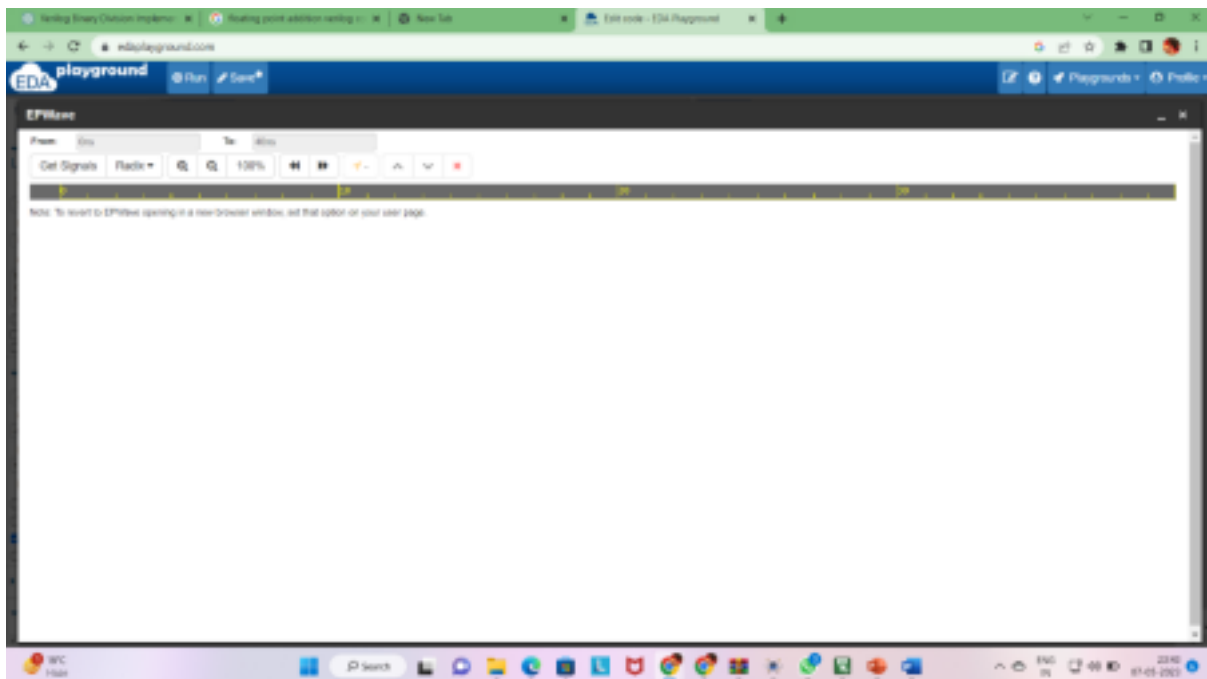

CARRY SELECT ADDER:

CODE:

```
module cfa_adder(a, b, cin, sum, cout);

input [3:0] a, b;

input cin;
output [3:0] sum;

output cout;
```

```

wire [3:0] cf;

// generate sum and carry for each bit
genvar i;
generate
for (i = 0; i < 4; i = i + 1) begin: ADDER_GEN
    carry_forward_adder cfa(.a(a[i]), .b(b[i]), .cin(cin), .cf(cf[i]), .sum(sum[i]));
assign cin = cf[i];
end
endgenerate

// output carry for MSB
assign cout = cf[3];
endmodule

// Carry forward adder module
module carry_forward_adder(a, b, cin, cf, sum);
    input a, b, cin;
    output cf, sum;

    assign sum = a ^ b ^ cin;
    assign cf = (a & b) | (a & cin) | (b & cin);
endmodule

```

TEST BENCH CODE:

```

module cfa_adder_tb;
    reg [3:0] a, b;
    reg cin;
    wire [3:0] sum;
    wire cout;

```

```
cfa_adder adder(.a(a), .b(b), .cin(cin), .sum(sum), .cout(cout));
```

```
initial begin
```

```
$dumpfile("cfa_adder_tb.vcd");
```

```
$dumpvars(0, cfa_adder_tb);
```

```
a = 4'b0000;
```

```
b = 4'b0000;
```

```
cin = 0;
```

```
#10 a = 4'b0001;
```

```
#10 b = 4'b0001;
```

```
#10 a = 4'b0011;
```

```
#10 b = 4'b0001;
```

```
#10 a = 4'b1111;
```

```
#10 b = 4'b0001;
```

```
#10 a = 4'b1001;
```

```
#10 b = 4'b0110;
```

```
#10 a = 4'b1010;
```

```
#10 b = 4'b0110;
```

```
#10 a = 4'b1111;
```

```
#10 b = 4'b1111;
```

```
#10 $finish;
```


end

always @(a, b, cin) begin


```
#5 $display("a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

end

endmodule

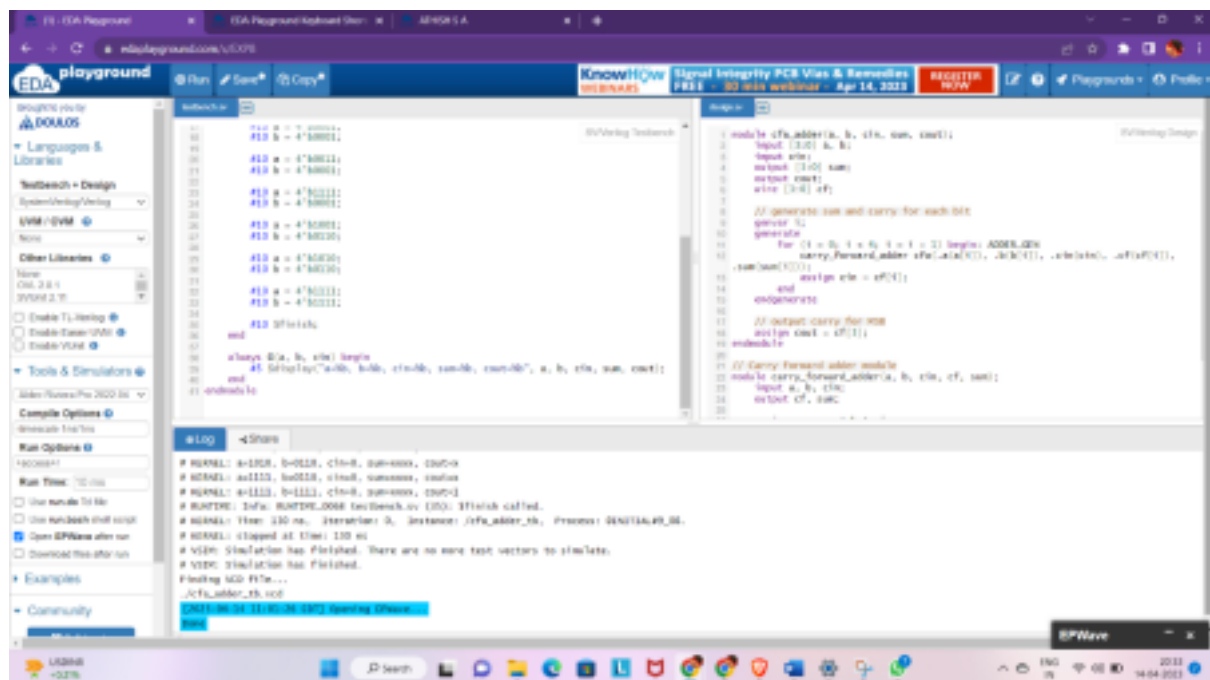

EPWAVE:

 

CARRY SAVE ADDER:

CODE:

```
module csa_4bit(a, b, c, sum, carry);
```

```
input [3:0] a, b, c;
```

```
output [3:0] sum;
```

```
output carry;
```

```
wire [3:0] temp_sum;
wire [3:0] temp_carry;

assign temp_sum = a ^ b ^ c;
assign temp_carry = (a & b) | (b & c) | (a & c);

assign sum = temp_sum;
assign carry = temp_carry[3];

endmodule
```

TEST BENCH CODE:

```
module csa_4bit_tb;

reg [3:0] a, b, c;
wire [3:0] sum;
wire carry;

csa_4bit dut(.a(a), .b(b), .c(c), .sum(sum), .carry(carry));

initial begin

$dumpfile("csa_4bit_tb.vcd");
$dumpvars(0, csa_4bit_tb);

a = 4'b0001;
b = 4'b0100;
```


c = 4'b1010;

#10;

a = 4'b1101;

b = 4'b1011;


c = 4'b0100;

#10;

\$finish;

end

endmodule

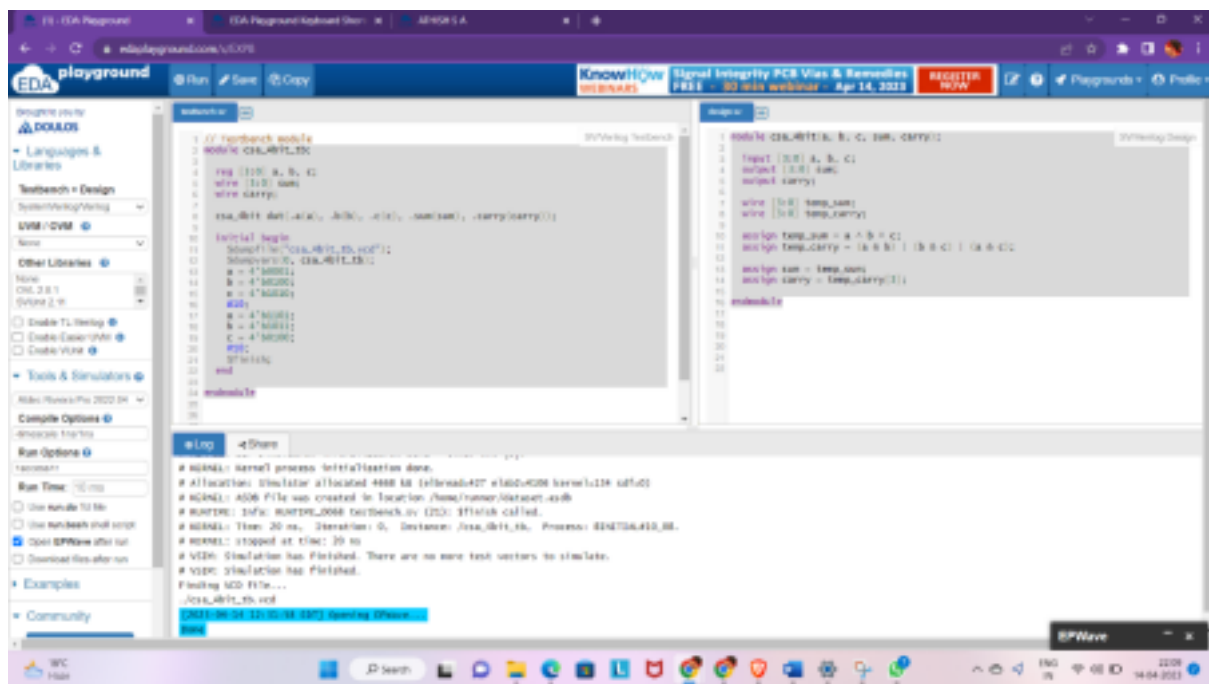

EP WAVE:



BINARY MULTIPLIER:

CODE:

```
module binary_multiplier(A, B, P);

    input [7:0] A, B;
    output reg [15:0] P;

    always @(*) begin
        P = A * B;
    end

endmodule
```

TEST BENCH CODE:

```
module binary_multiplier_tb;

    reg [7:0] A, B;
    wire [15:0] P;

    binary_multiplier dut(.A(A), .B(B), .P(P));

    initial begin
        $dumpfile("binary_multiplier_tb.vcd");
        $dumpvars(0, binary_multiplier_tb);

        A = 8'b01010101;
        B = 8'b00110011;

        #10;


        A = 8'b11110000;
        B = 8'b00001111;

        #10;


        $finish;
    end

end
```

endmodule

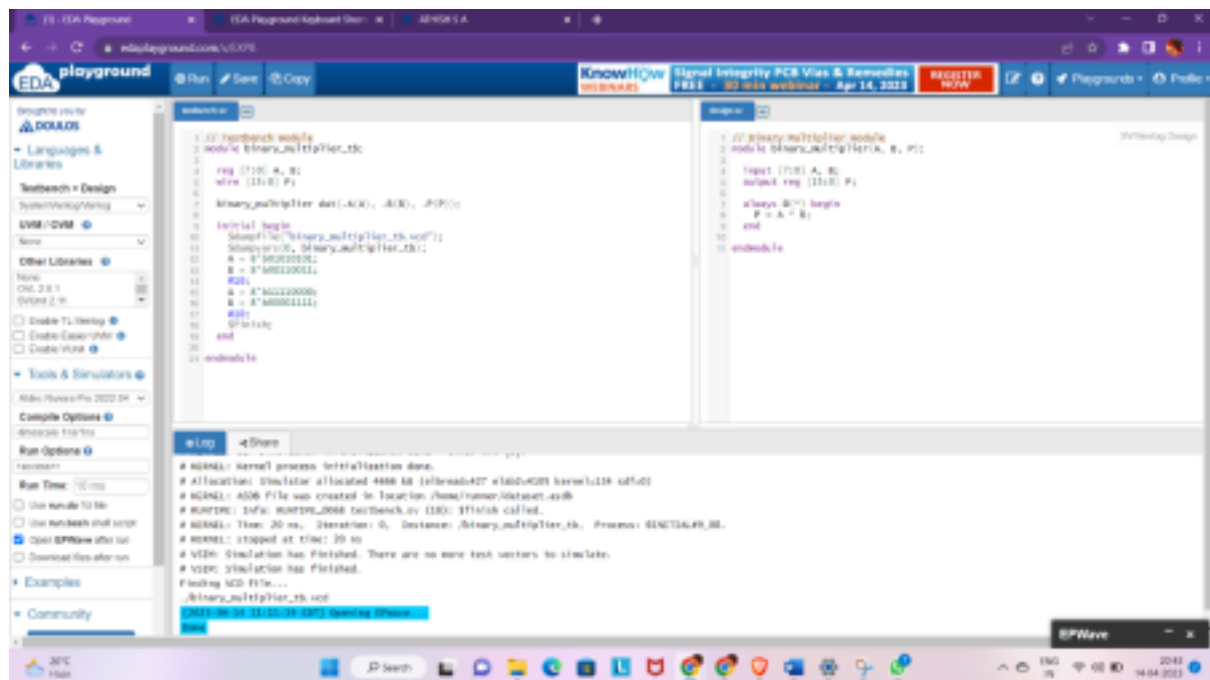

EP WAVE:

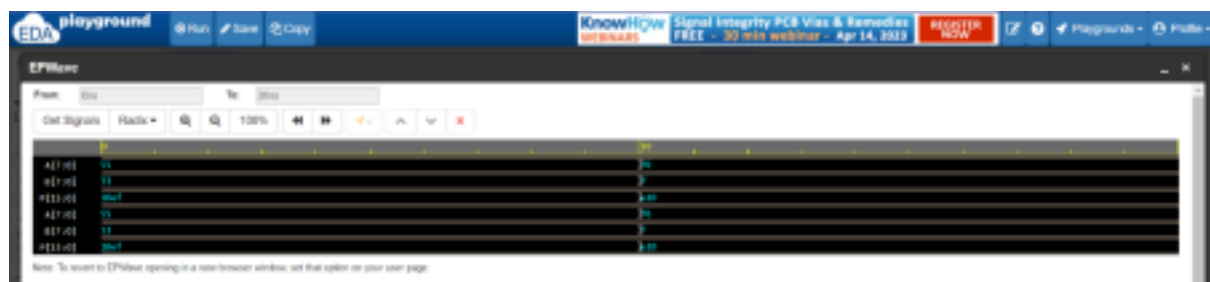

BOOTHS MULTIPLIER:

CODE:

```
module booths_multiplier(A, B, P);
```

```
input [7:0] A, B;
output reg [15:0] P;
```

```
reg [7:0] A_reg, B_reg;
```

```
reg [1:0] count;
```

```
reg signed [15:0] P_reg;
```

```

always @(*) begin
A_reg = A;
B_reg = B;
count = 0;
P_reg = 0;
repeat(8) begin
if (B_reg[0] == 1) begin
P_reg = P_reg + (A_reg << count);
end
else if (B_reg[1] == 1) begin
P_reg = P_reg + (A_reg << count); P_reg =
P_reg + (A_reg << (count + 1)); end
count = count + 2;
B_reg = {B_reg[6:0], B_reg[7]};
end
P = P_reg;
end

endmodule

```

TEST BENCH CODE:

```

module booths_multiplier_tb;

reg [7:0] A, B;
wire [15:0] P;


booths_multiplier dut(.A(A), .B(B), .P(P));

initial begin

```

endmodule



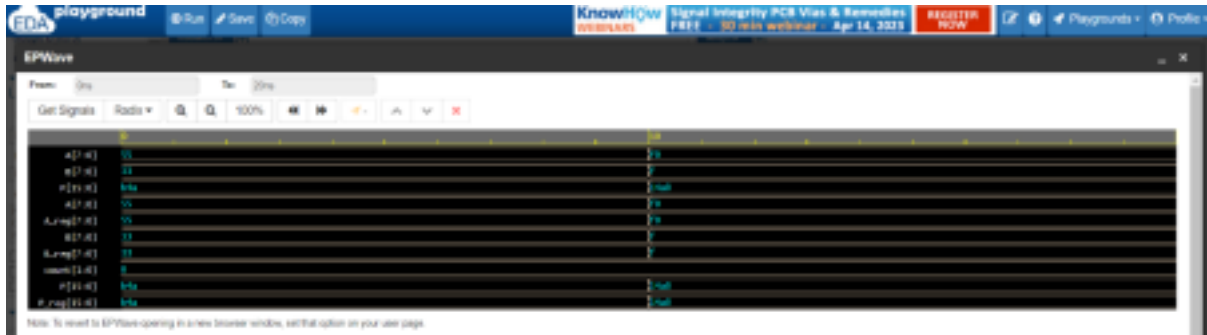

WALLACE MULTIPLIER:

CODE:

```
module wallace_multiplier(A, B, P);
```

```
    input [7:0] A, B;
```

```
    output reg [15:0] P;
```

```
    reg [7:0] A_reg, B_reg;
```

```
    wire [23:0] P_intermediate [7:0];
```

```
    wire [23:0] P_partial_sum [3:0];
```

```
    reg [15:0] P_reg;
```

```
    assign P_intermediate[0] = {A_reg, 8'b0};
```

```
    assign P_intermediate[1] = {A_reg, 8'b0} + {B_reg, 7'b0};
```

```
    assign P_intermediate[2] = {A_reg, 8'b0} + {B_reg[1:0], 6'b0};
```

```
    assign P_intermediate[3] = {A_reg, 8'b0} + {B_reg[2:0], 5'b0};
```

```
    assign P_intermediate[4] = {A_reg, 8'b0} + {B_reg[3:0], 4'b0};
```

```
    assign P_intermediate[5] = {A_reg, 8'b0} + {B_reg[4:0], 3'b0};
```

```
    assign P_intermediate[6] = {A_reg, 8'b0} + {B_reg[5:0], 2'b0};
```

```
    assign P_intermediate[7] = {A_reg, 8'b0} + {B_reg[6:0], 1'b0};
```

```
    assign P_partial_sum[0] = P_intermediate[0] + P_intermediate[1];
```

```
    assign P_partial_sum[1] = P_intermediate[2] + P_intermediate[3];
```

```
assign P_partial_sum[2] = P_intermediate[4] + P_intermediate[5];
```

```
assign P_partial_sum[3] = P_intermediate[6] + P_intermediate[7];
```

```
always @(*) begin
```

```
  A_reg = A;
```

```
  B_reg = B;
```

```
  P_reg = 0;
```

```
  for (int i = 0; i < 4; i = i + 1) begin
```

```
    P_reg = P_reg + (P_partial_sum[i] << (3*i));
```

```
  end
```

```
  P = P_reg;
```

```
end
```

```
endmodule
```

TEST BENCH CODE:

```
module wallace_multiplier_tb;
```

```
  reg [7:0] A, B;
```

```
  wire [15:0] P;
```

```
  wallace_multiplier dut(.A(A), .B(B), .P(P));
```

```
  initial begin
```

```
    $dumpfile("wallace_multiplier_tb.vcd");
```

```
    $dumpvars(0, wallace_multiplier_tb);
```

```
    A = 8'b01010101;
```

```
    B = 8'b00110011;
```

```
    #10;
```

```
    A = 8'b11110000;
```


```
    B = 8'b00001111;
```

#10;

\$finish;

end

endmodule

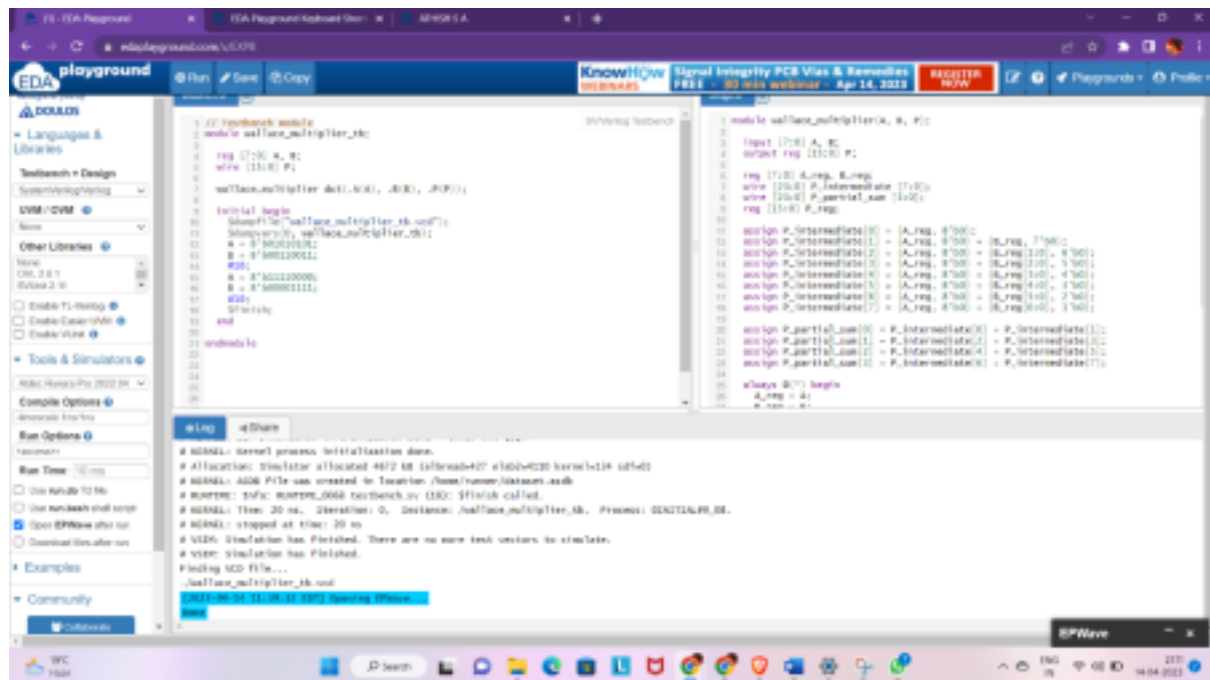

EPWAVE:



DIVISION CIRCUIT:

CODE:

```
module division_circuit(dividend, divisor, quotient);
```



```

input [7:0] dividend, divisor;
output reg [7:0] quotient;

reg [7:0] remainder;

always @(*) begin
    quotient = 0;
    remainder = dividend;
    for (int i = 0; i < 8; i = i + 1) begin
        quotient = quotient << 1;
        remainder = remainder << 1;
        if (remainder >= divisor) begin
            quotient[i] = 1;
            remainder = remainder - divisor;
        end
    end
end
endmodule

```

TEST BENCH CODE:

```

module division_circuit_tb;

    reg [7:0] dividend, divisor;
    wire [7:0] quotient;

    division_circuit dut(.dividend(dividend), .divisor(divisor), .quotient(quotient));

    initial begin
        $dumpfile("division_circuit_tb.vcd");
    end
endmodule

```

```
$dumpvars(0, division_circuit_tb);
```

```
dividend = 8'b11011010;
```

```
divisor = 8'b00101100;
```

```
#10;
```

```
dividend = 8'b11110000;
```

```
divisor = 8'b00001111;
```

```
#10;
```

```
$finish;
```

```
end
```

```
endmodule
```



EPWAVE:

