

Name : ATHISH S A

Roll No: B21EC040

GATES IMPLEMENTATION USING VERILOG

1. Not Gate

Gate Level Modeling


```
module not_gate(c,a);  
input a;  
output c;  
not (c,a);  
endmodule
```

Data Flow Modeling

```
module not_data(c,a);  
input a;  
output c;  
assign c=~a;  
endmodule
```

Behavioral Modeling
 
```
module not_beh(c,a);  
input a;  
output c;  
reg c;  
always@(a)  
begin  
if (a==0)  
c=1;  
else  
c=0;  
end  
endmodule
```



2. NOR Gate

Gate Level Modeling

```
module nor_gate(c,a,b);
input a,b;
output c;
nor (c,a,b);
endmodule
```

Data Flow Modeling

```
module nor_data(c,a,b);
input a,b;
output c;
assign c=~(a|b);
endmodule
```

Behavioral Modeling

```
module nor_beh(c,a,b);
input a,b;
output c;
```

```

reg c;
always@(a,b)

begin
if (a==0 & b==0)
c=1;
else
c=0;
end
endmodule

```



3. And Gate

Gate Level Modeling

```

module
and_gate(c,a,b); input
a,b;
output c;
and (c,a,b);
endmodule

```

Data Flow Modeling

```

module
and_data(c,a,b); input
a,b;
output c;
assign c = a & b;

```

```
endmodule
```

Behavioral Modeling

```
module  
and_beh(c,a,b); input  
a,b;  
output c;  
reg c;  
always@(a,b)  
  
begin  
if (a==0|b==0)  
c=0;  
else  
if(a==0|b==1)  
c=0;  
else  
if(a==1|b==0)  
c=0;  
else  
c=1;  
end  
endmodule
```



4. Or Gate

Gate Level Modeling


```
module or_gate(c,a,b);  
input a,b;  
output c;  
or (c,a,b);  
endmodule
```

Data Flow Modeling

```
module or_data(c,a,b);  
input a,b;  
output c;  
assign c=a|b;  
endmodule
```

Behavioral Modeling

```
module or_beh(c,a,b);  
input a,b;  
output c;  
reg c;  
always@(a,b);  
  
initial  
  
begin  
if (a==0|b==0)  
c=0;  
else if(a==0|b==1)  
c=0;  
else if(a==1|b==0)  
c=0;  
else  
c=1;  
end  
endmodule
```

 

5. NAND Gate

Gate Level Modeling

```
module nand_gate(c,a,b);
input a,b;

output c;

nand (c,a,b);

endmodule
```

Data Flow Modeling

```
module
nand_data(c,a,b); input
a,b;

output c;

assign c =~(a&b);

endmodule
```

Behavioral Modeling

```
module
nand_beh(c,a,b); input
a,b;

output c;

reg c;


always@(a,b)
```

```
begin
```

```

if (a==1 & b==1)
c=0;
else
c=1;
end
endmodule

```

 

6. XOR Gate

Gate Level Modeling

```

module xor_gate(c,a,b);
input a,b;
output c;
xor (c,a,b);
endmodule

```

Data Flow Modeling

```

module xor_data(c,a,b);
input a,b;
output c;
assign c=(a^b);
endmodule

```

Behavioral Modeling

```

module xor_beh(c,a,b);
input a,b;
output c;
reg c;

```

```

always@(a,b)
begin
if (a==0 & b==0)
c=0;
else if (a==1 & b==1)
c=0;
else
c=1;
end
endmodule

```



7. XNOR Gate

Gate Level Modeling

```

module xnor_gate(c,a,b);
input a,b;
output c;
xnor (c,a,b);
endmodule

```

Data Flow Modeling

```

module

```



```
xnor_data(c,a,b); input
```

```
a,b;
```

```
output c;
```

```
assign c=~(a^b);
```

```
endmodule
```

Behavioral Modeling

```
module
```

```
xnor_beh(c,a,b); input
```

```
a,b;
```

```
output c;
```

```
reg c;
```

```
always@(a,b)
```

```
begin
```

```
if (a==0 & b==0)
```

```
c=1;
```

```
else if (a==1 &
```

```
b==1) c=1;
```

```
else
```

```
c=0;
```

```
end
```

```
endmodule
```



8. Half Adder

Gate Level Modeling

```
module halfadder_gate (s,c,a,b);  
    input a,b;  
    output s,c;  
    xor(s,a,b);  
    and(c,a,b);  
endmodule
```

Data Flow Modeling

```
module halfadder_data (s,c,a,b);  
    input a,b;  
    output s,c;  
    assign s=a^b;  
    assign c=a&b;  
endmodule
```

Behavioral Modeling

```
module halfadder_beh(s,c,a,b);  
    input a,b;  
    output s,c;  
    reg s,c;  
    always@(a,b)
```

```
begin  
    if (a==b)  
        begin  
            s=0;  
            c=b;  
        end  
end
```

```

else
begin
s=1;
c=0;
end
end
endmodule

```



9. Full Adder

Gate Level Modeling

```

module
fulladder_gate(s,c,a,b,cin); input
a,b,cin;
output s,c;
wire i1,i2,i3;
xor (i1,a,b);
and (i2,a,b);
xor (s,i1,cin);
and (i3,i1,cin);
or (c,i2,i3);
endmodule

```

Data Flow Modeling

```

module
fulladder_data(s,c,a,b,cin); input
a,b,cin;
output s,c;

```

```
wire i1,i2,i3;  
assign s=i1^cin;  
assign i2=a&b;  
assign i1=a^b;  
assign i3=cin&i1;  
assign c=i2|i3;  
endmodule
```

Behavioral Modeling

```
module  
fulladder_beh(s,c,a,b,cin); input  
a,b,cin;  
output s,c;  
reg s,c;  
always@(a,b,cin)
```

```
begin  
if (a==b)  
begin  
s=cin;  
c=b;  
end  
else  
begin  
s=~cin;  
c=cin;  
end  
end  
endmodule
```



10. 4:1 MUX

Gate Level Modeling

```
module mux_gate(a,b,c,d,select0,select1,y);
input a,b,c,d,select0,select1;
output y;
wire i1,i2,i3,i4,i5,i6;
not (i1,select0);
not (i2,select1);
and (i3,i1,i2,a);
and (i4,i1,select1,b);
and (i5,select0,i2,c);
and (i6,select0,select1,d);
or (y,i3,i4,i5,i6);
endmodule
```

Data Flow Modeling

```
module
mux_data(a,b,c,d,select0,select1,y); input
a,b,c,d,select0,select1;
output y;
wire i1,i2,i3,i4,i5,i6;
assign i1=~select0;
assign i2=~select1;
assign i3=i1&i2&a;
```

```

assign i4=i1&select1&b;
assign i5=select0&i2&c;
assign i6=select0&select1&d;
assign y=i3|i4|i5|i6;
endmodule

Behavioral Modeling


module mux_beh(a,b,c,d,select0,select1,y);
input a,b,c,d,select0,select1;
output y;
reg y;
always @ (a or b or c or d or select0 or select1)

```

```


begin
if (select0 == 0 & select1 ==0)
y = a;
else if (select0 == 0 & select1 ==1)
y = b;
else if (select0 == 1 & select1 ==0)
y = c;
else
begin
y = d;
end
end
endmodule

```

 


11. 4:2 Encoder

```
module encoder_4_2(a,b,c,d,x,y);  
    output x,y;  
    input a,b,c,d;  
    assign x = b | d;  
    assign y = c | d;  
endmodule
```

 

 12. D-FF

```
module d_ff_beh(D,CLK,RST,Q,Qbar);  
    output Q,Qbar;  
    input D,CLK,RST;  
    reg Q;  
    always @(posedge CLK)  
  
    begin // positive-edge triggered  
        if (!RST) // synchronous reset, active low  
            Q <= 1'b0;  
        else  
            Q <= D; // characteristic equation  
        end  
    assign Qbar = ~ Q ;  
endmodule
```




13. JK-FF

```

module jk_ff_beh(J,K,CLK,RST,Q,Qbar);
output Q,Qbar;
input J,K,CLK,RST;
reg Q;
always @(posedge CLK)

begin // positive-edge triggered
if (!RST) // synchronous reset, active low
Q <= 1'b0;
else
Q <= (J & ~Q)|(~K & Q); // characteristic equation
end
assign Qbar = ~ Q ;
Endmodule

```

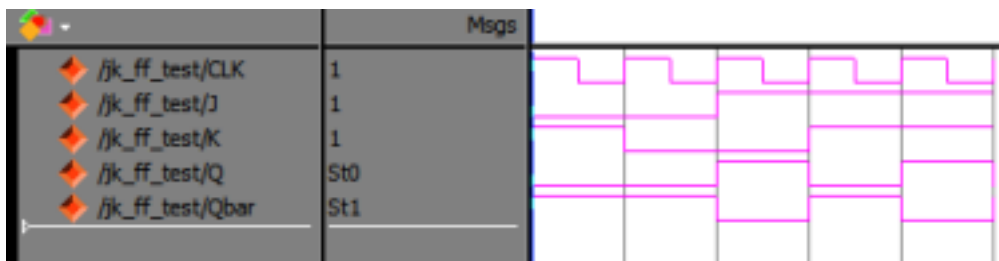

14. SR-FF

```

module sr_ff_beh(S,R,CLK,RST,Q,Qbar);
output Q,Qbar;
input S,R,CLK,RST;
reg Q;
always @(posedge CLK)


```



```

begin // positive-edge triggered
if (!RST) // synchronous reset, active low
Q <= 1'bo;
else
Q <= (S)|(~R & Q); // characteristic equation
end
assign Qbar = ~ Q ;
endmodule

```

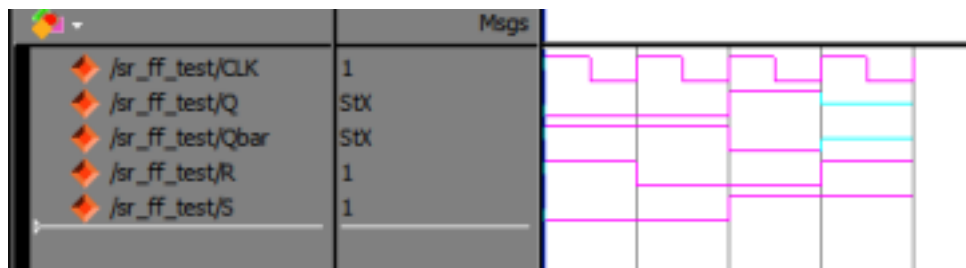

15. T-FF

```

module t_ff_beh(T,CLK,RST,Q,Qbar);
output Q,Qbar;
input T,CLK,RST;
reg Q;
always @(posedge CLK)

begin // positive-edge triggered
if (!RST) // synchronous reset, active low
Q <= 1'bo;
else
Q <= T^Q;
//Q <= (~T&Q)|(T&~Q); // characteristic equation
end
assign Qbar = ~ Q ;
endmodule;

```

